

$\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 100 \mu A/V^2$, NMOS $V_{TH} = 0.4 V$, PMOS $V_{TH} = -0.4 V$,

7.7 We wish to design the stage in Fig 7.40 for a drain current of 0.5 mA. If $W/L = 50/0.18$, calculate the value of R_1 and R_2 such that these resistors carry a current equal to one-tenth of I_{D1} .

 


Fig. 7.40

7.17 We wish to design a stage of Fig 7.50 for a voltage gain of 5 with $W/L \leq 20/0.18$. Determine the required R_D if the power dissipation must not exceed 1 mW.

 


Fig. 7.50

7.21 Explain which one of the topologies shown in Fig. 7.54 is preferred.

 


Fig. 7.54

7.23 The CS stage shown in Fig. 7.56 must achieve a gain of 7. If $(W/L)_2 = 2/0.18$, compute the required value of $(W/L)_1$.

 


Fig. 7.56