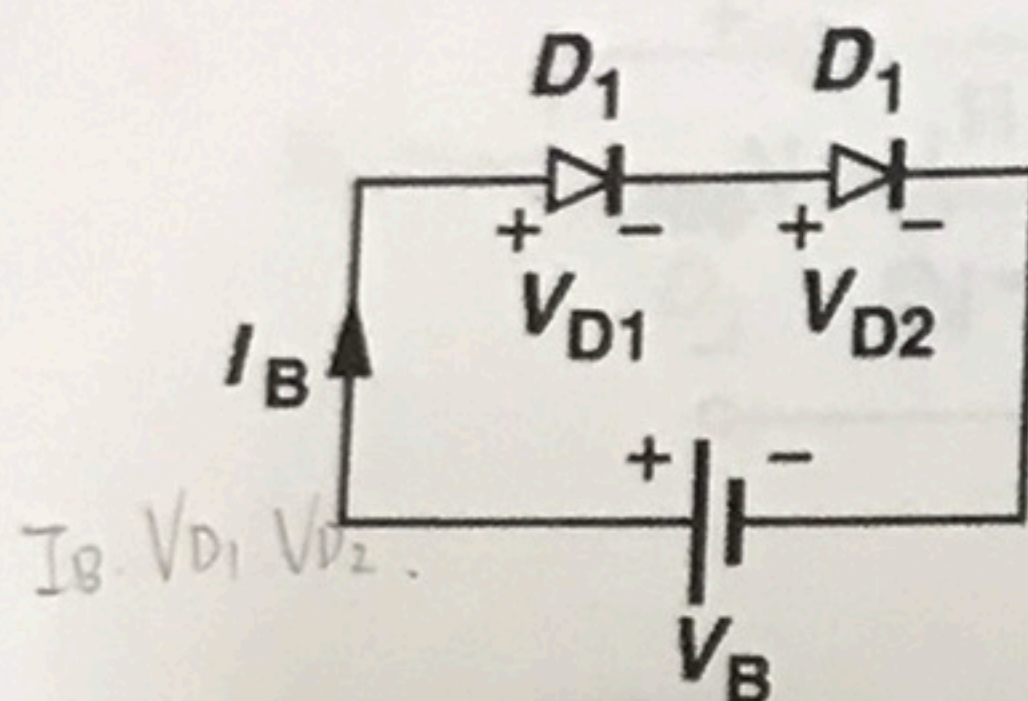


Name: 艾利

ID# B083040004

1. (15%) Two diodes with reverse saturation currents of I_{S1} and I_{S2} placed series. Calculate I_B , V_{D1} , and V_{D2} in terms of V_B , I_{S1} , and I_{S2} . $I_D = I_S \exp(V_D/V_T)$ $V_T = 26\text{mV}$

 I_B, V_{D1}, V_{D2} V_B, I_{S1}, I_{S2}

$$I_B = I_{D1} = I_{D2}$$

$$V_B = V_{D1} + V_{D2}$$

$$= V_T \ln \frac{I_B}{I_{S1}} + V_T \ln \frac{I_B}{I_{S2}}$$

$$= V_T \ln \left(\frac{I_B^2}{I_{S1} I_{S2}} \right)$$

$$I_B = e^{\frac{V_B}{2V_T}} \sqrt{I_{S1} I_{S2}}$$

$$= e^{\frac{V_B}{2V_T}} \sqrt{I_{S1} I_{S2}} \#$$

$$I_B = I_{S1} \exp\left(\frac{V_{D1}}{V_T}\right)$$

$$\frac{I_B}{I_{S1}} = \exp\left(\frac{V_{D1}}{V_T}\right)$$

$$\ln\left(\frac{I_B}{I_{S1}}\right) = \frac{V_{D1}}{V_T}$$

$$V_{D1} = V_T \ln\left(\frac{I_B}{I_{S1}}\right)$$

$$= 0.026 \times \ln\left(\frac{e^{\frac{V_B}{2V_T}} \sqrt{I_{S1} I_{S2}}}{I_{S1}}\right)$$


$$= 0.026 \times \left(\ln e^{\frac{V_B}{2V_T}} + \ln \frac{\sqrt{I_{S1} I_{S2}}}{I_{S1}} \right)$$

$$= 0.026 \left(\frac{V_B}{0.026} + \ln \sqrt{\frac{I_{S2}}{I_{S1}}} \right)$$

$$= \frac{V_B + 0.026 \ln \sqrt{\frac{I_{S2}}{I_{S1}}}}{2} \#$$

$$V_{D2} = \frac{V_B + 0.026 \ln \sqrt{\frac{I_{S1}}{I_{S2}}}}{2} \#$$

2. (15%) Determine the value of R_1 such that R_1 carries 0.5mA. Assume $I_S = 5 \times 10^{-16}$ A for each diode.

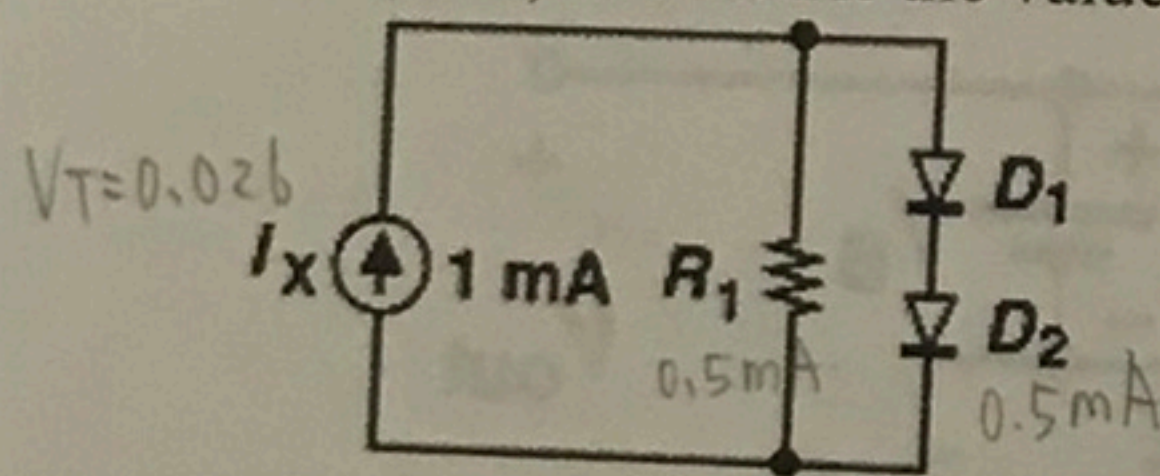 $V_T = 0.026$ $I_X = 1\text{mA}$ R_1 0.5mA 0.5mA

$$I_{D1} = I_{D2} = 1 - 0.5 = 0.5\text{mA}$$

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right)$$

$$0.5 \times 10^{-3} = 5 \times 10^{-16} \times e^{\frac{V_D}{0.026}}$$

$$e^{\frac{V_D}{0.026}} = \frac{5 \times 10^{-4}}{5 \times 10^{-16}} = 10^{12}$$

$$\frac{V_D}{0.026} = \ln 10^{12}$$

$$V_D = 0.026 \times \ln 10^{12}$$

$$= 0.026 \times 27.63$$

$$= 0.71838$$

$$= 0.7\text{V}$$

$$V_{R1} = V_{D1} + V_{D2}$$

$$= 0.7 \times 2$$


$$= 1.4$$

$$R_1 = \frac{1.4}{0.5 \times 10^{-3}}$$

$$= \frac{2.8}{10^{-3}}$$

$$= 2800 \Omega \#$$

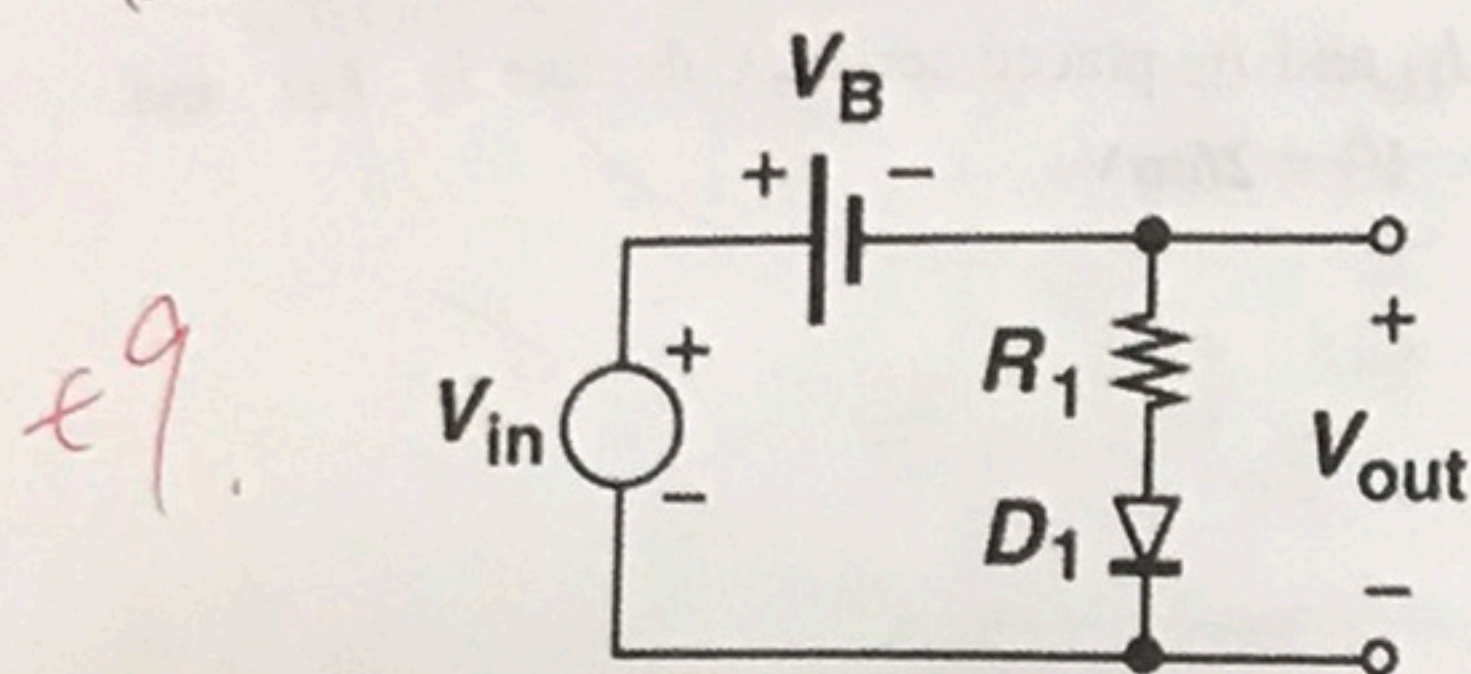3. (10%) Plot the input/output characteristics of the circuit shown below using an ideal model for the diode.
(Assume $V_B = 2V$).



D_1 off



$$V_{out} = V_{in} - V_B$$

$$= V_{in} - 2$$

D_1 on

$$V_{out} = V_{in} - V_B$$

$$= V_{in} - 2$$

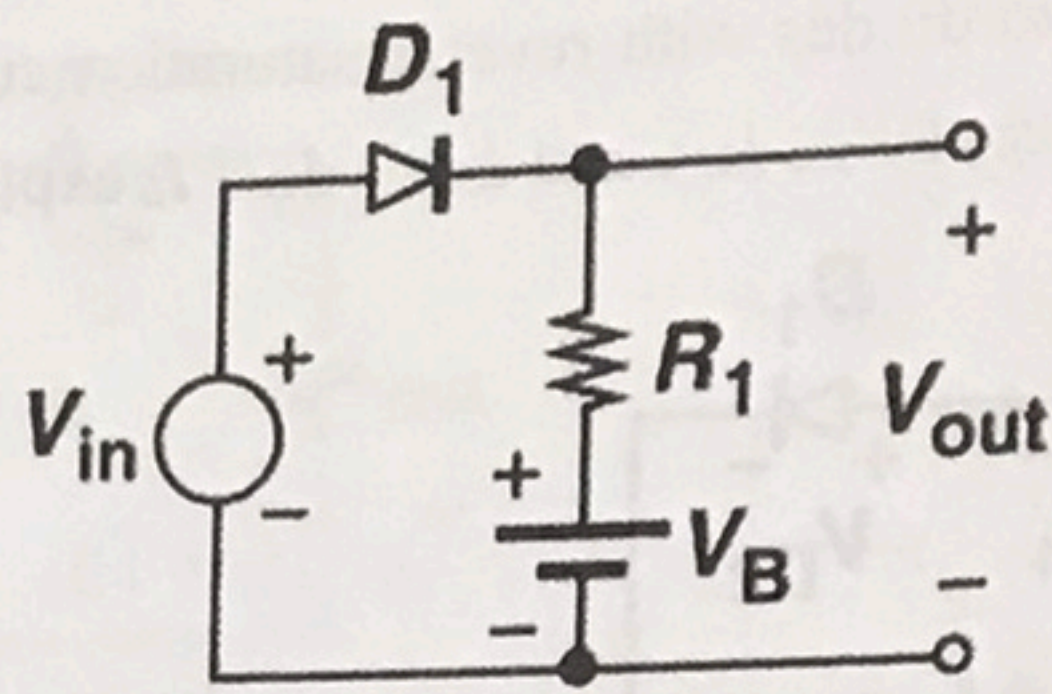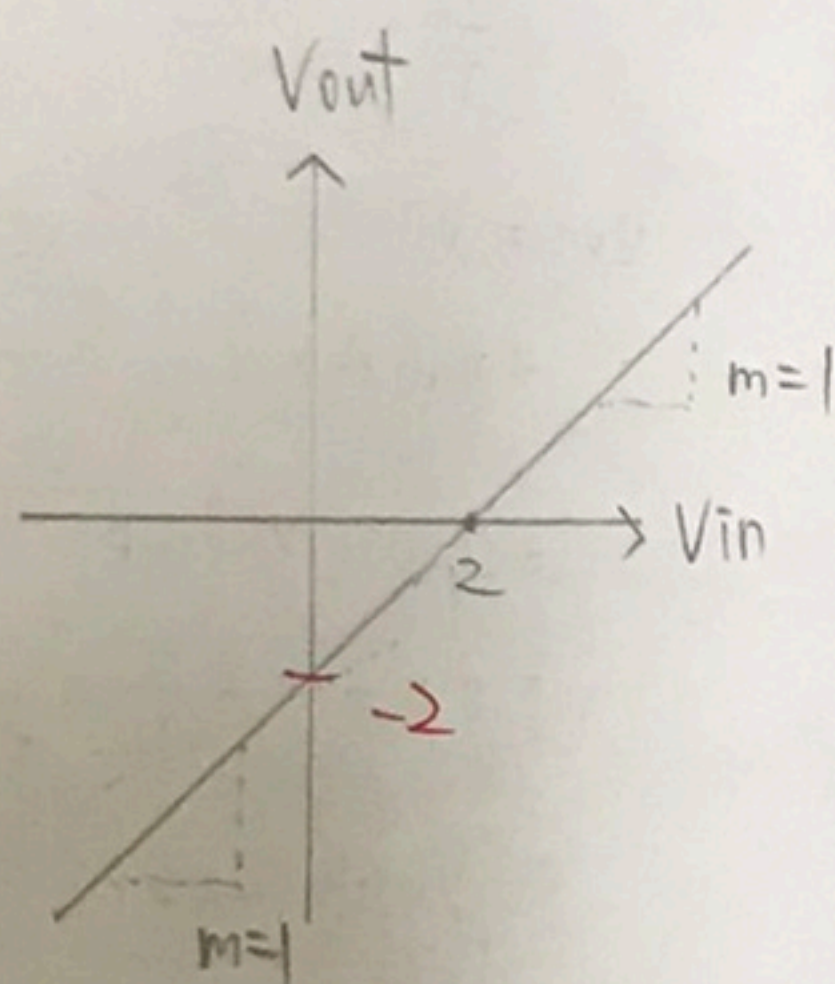


D_1 off


$$V_{out} = V_B = 2V$$

D_1 on

$$V_{out} = V_{in}$$

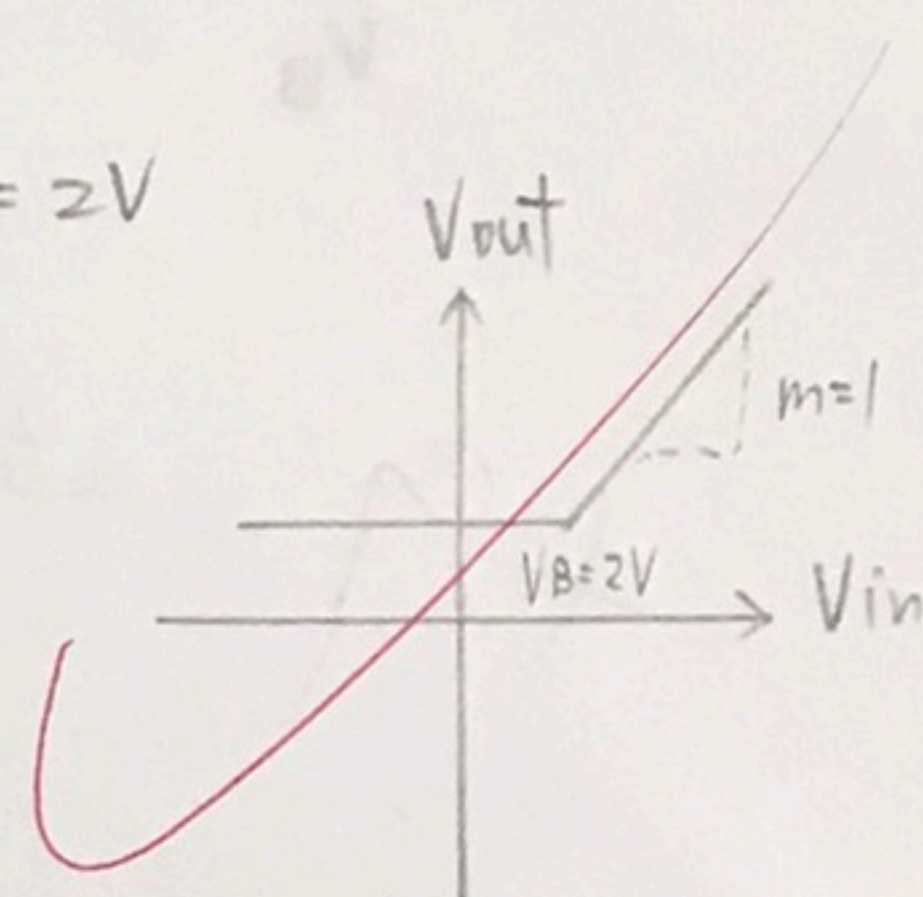

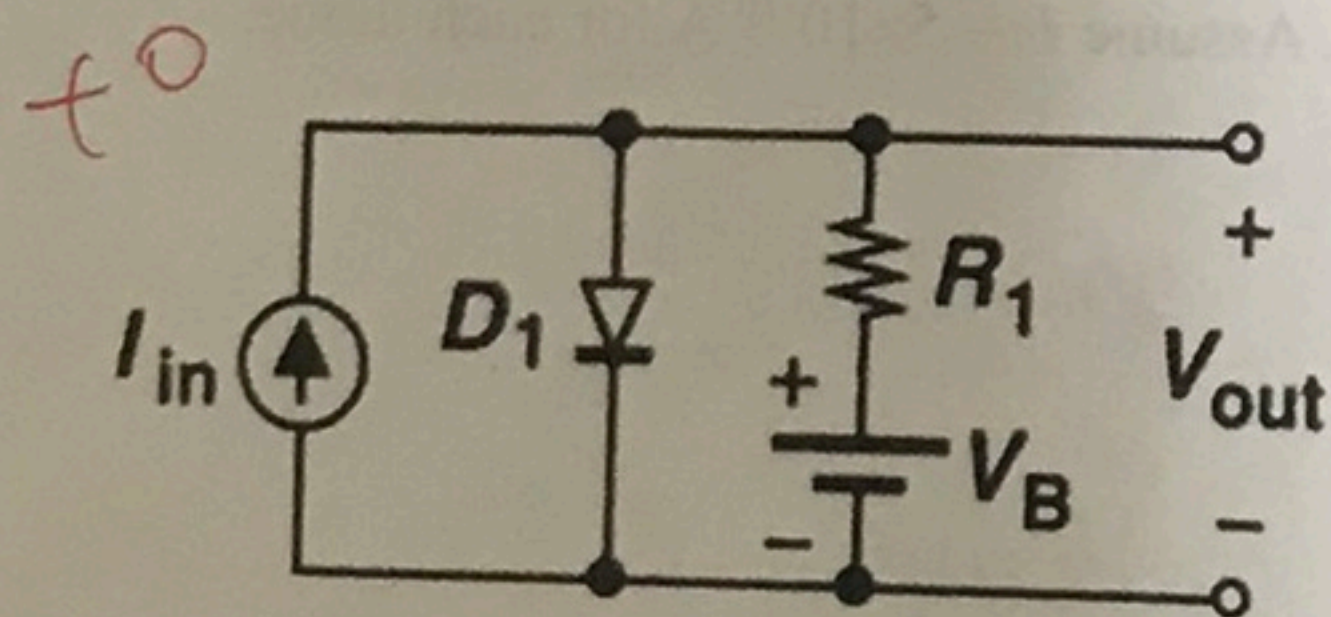4. (10%) Assume constant voltage diode model, plot I_{R1} as a function of I_{in} for the circuits shown below.
(Assume $V_B = 2V$).



D_1 off

$$I_{in} = I_{R1}$$



D_1 on

$$V_{D,on} = V_{R1} + V_B$$

$$V_{D,on} = I_{R1} R_1 + V_B$$

$$I_{R1} = \frac{V_{D,on} - V_B}{R_1}$$

$$= \frac{V_{D,on} - 2}{R_1}$$

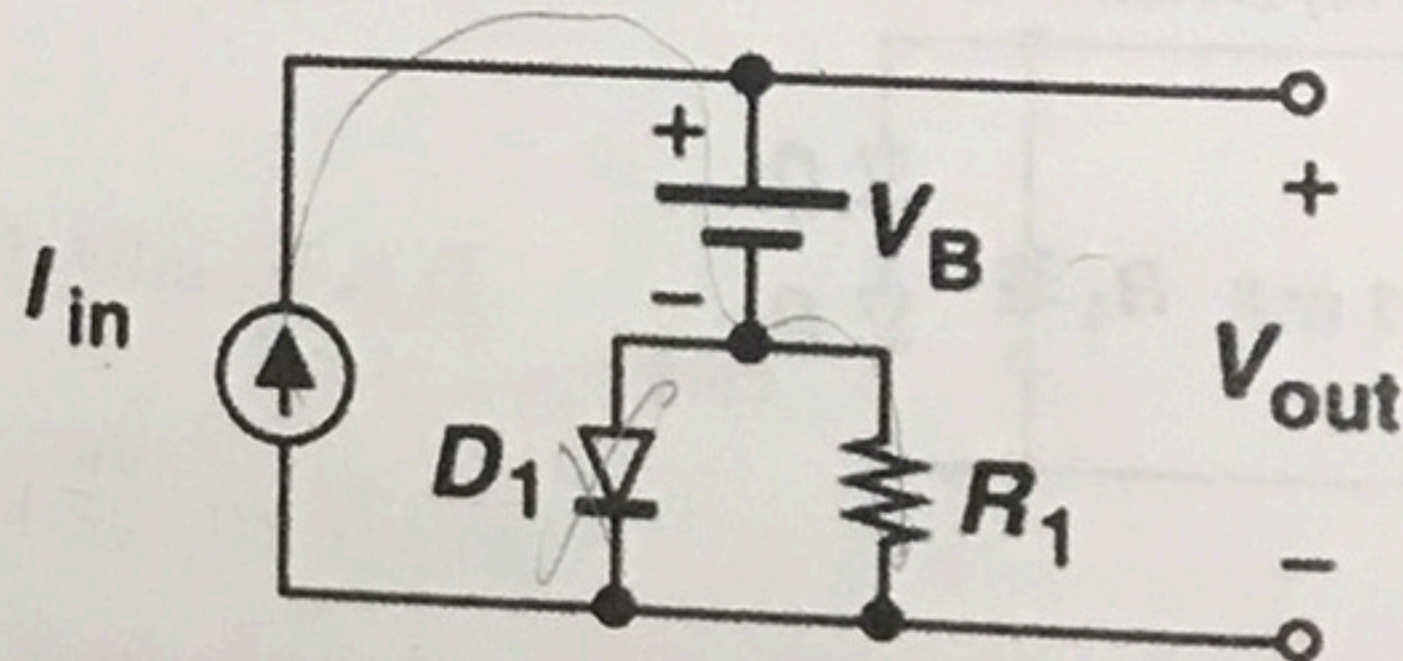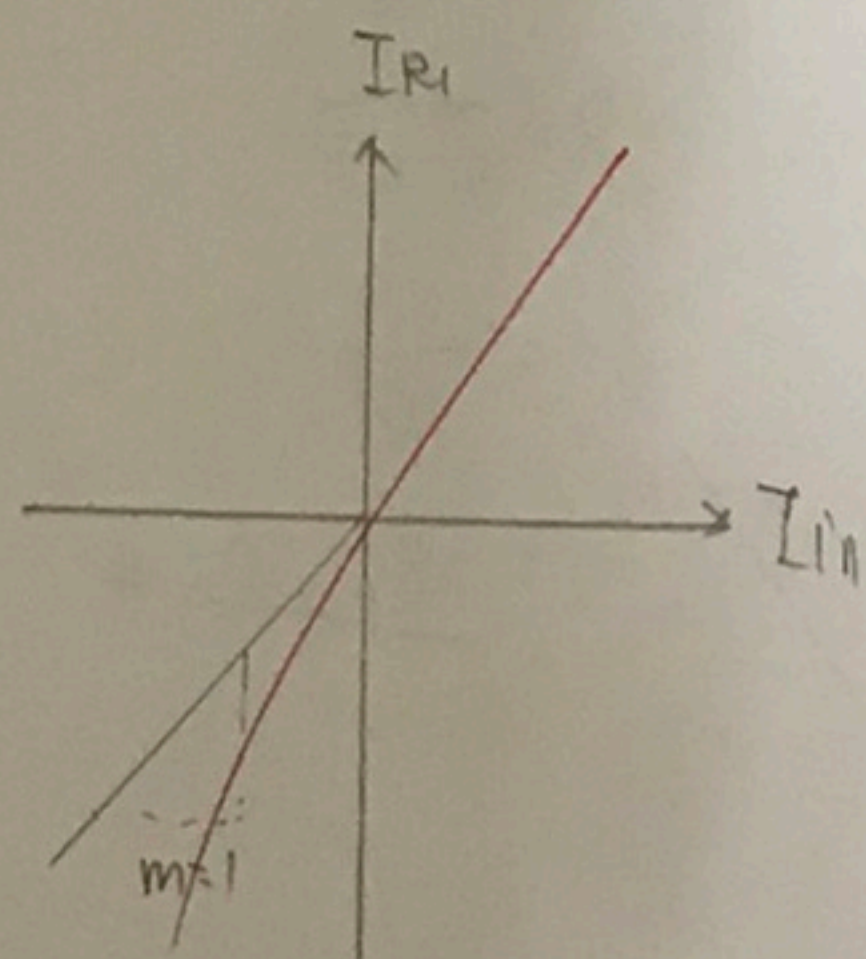


D_1 off


$$I_{in} = I_{R1}$$

D_1 on

$$V_{D,on} = I_{R1} R_1$$

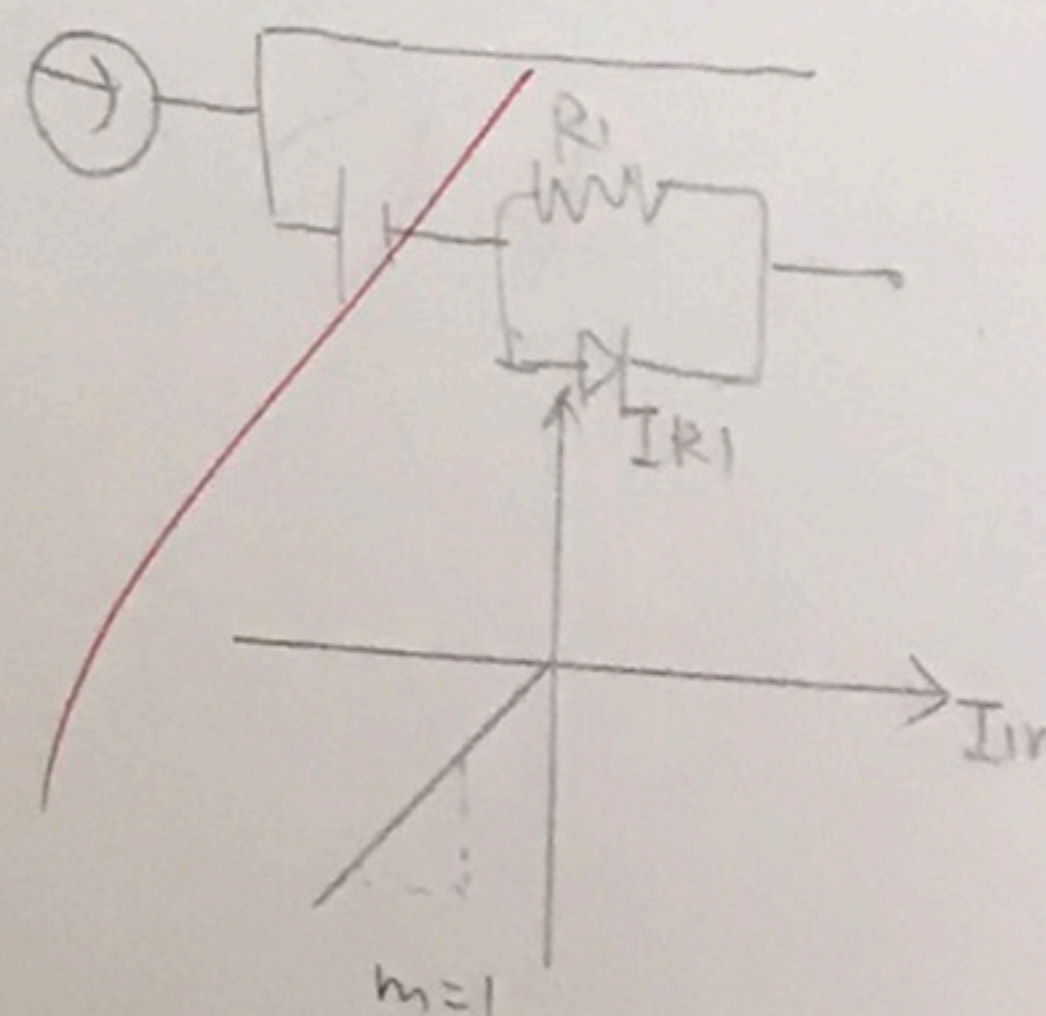

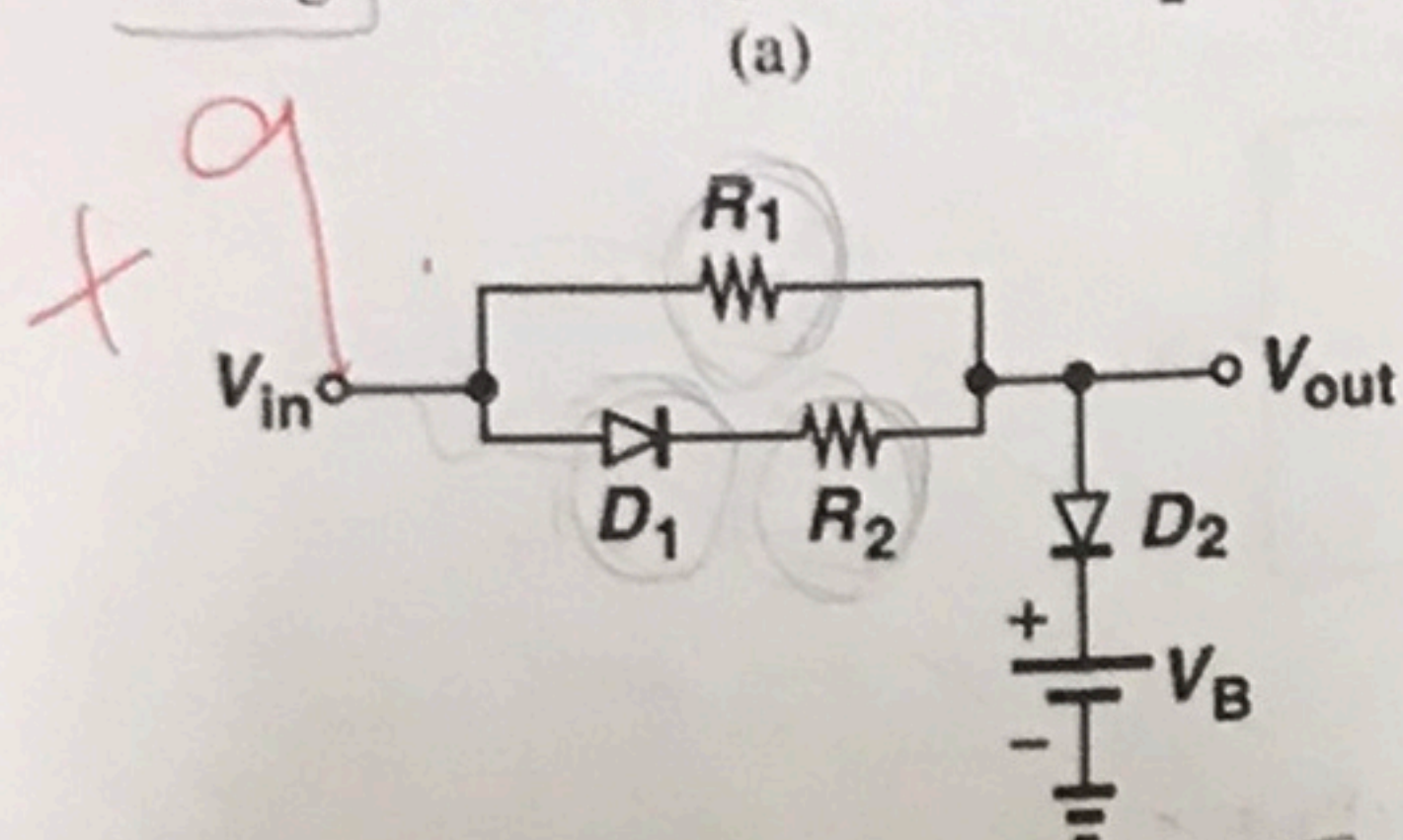5. (15%) Plot the input/output characteristics of the circuit illustrated in Fig. 3.76 assuming a constant voltage model and $V_B = 2$ V.



$V_{in} \rightarrow -\infty$, D_1 off, D_2 off

$V_{in} = V_{out}$

$V_{in} \rightarrow \infty$, D_1 on, D_2 off

$V_{D, on} + V_{R2} = V_{R1}$

$V_{out} = V_{in} - V_{D, on} - V_{R2}$

$= V_{in} - V_{R1} + V_{R2} - V_{R2}$



$= V_{in} - V_{R1}$

D_1 on, D_2 on

$V_{in} = V_{D1} + V_{B1} + V_{D2} + V_B$

$V_{out} = V_{D2} + V_B$

$= V_{in} - V_{D1} + V_{R2}$

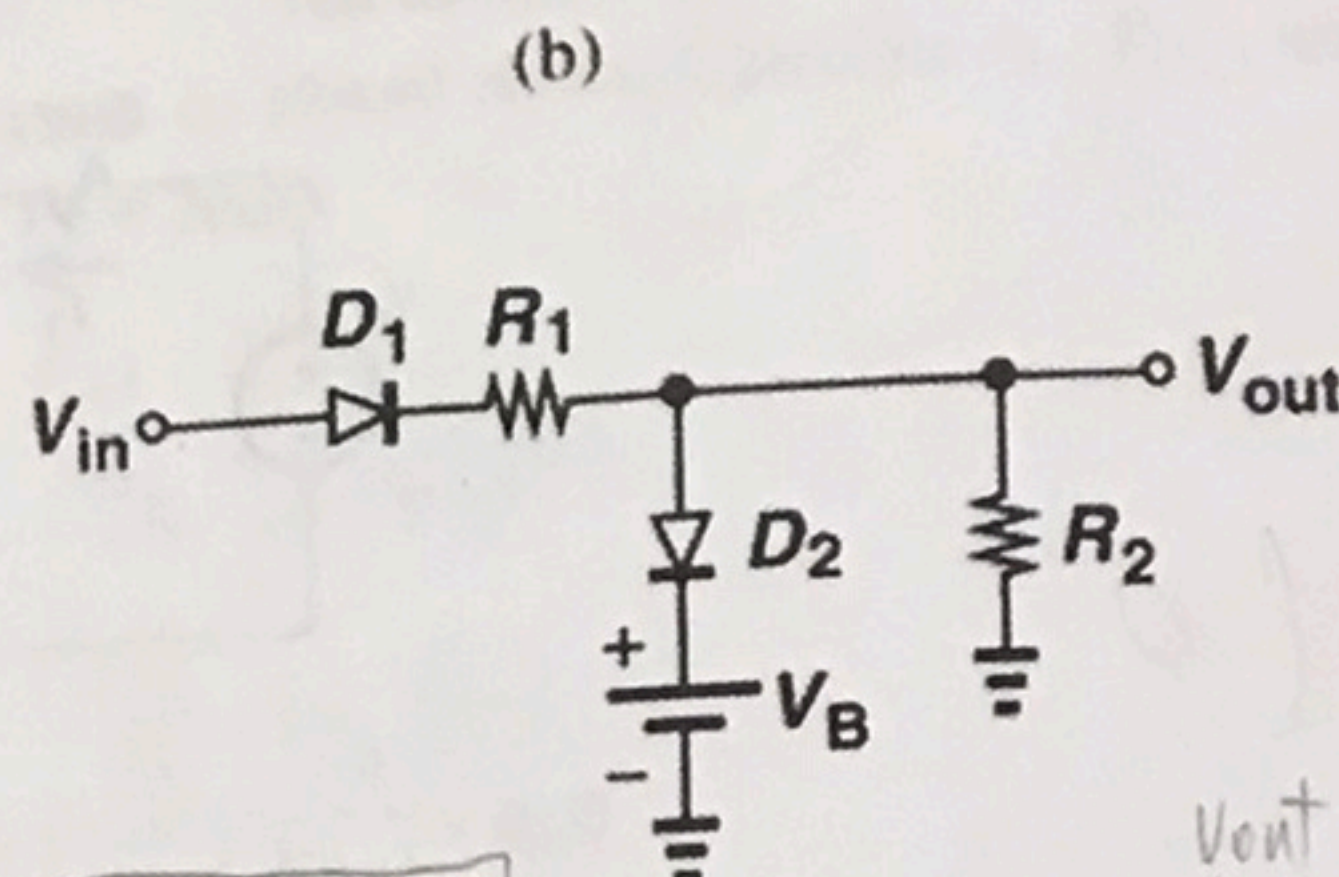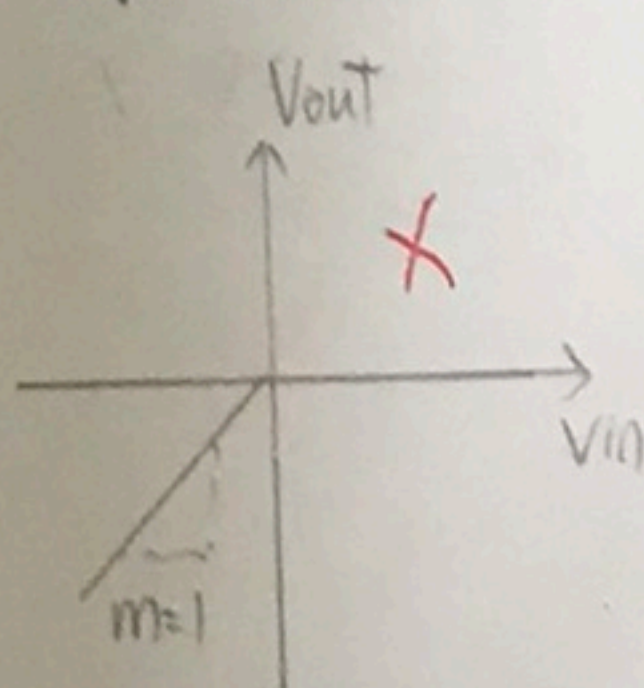

D_1 off, D_2 off

$V_{in} = V_{out}$


D_1 on, D_2 off

$V_{in} = V_{D1, on} + V_{R1} + V_{R2}$


$V_{out} = V_{R2}$

$= V_{in} - V_{D1, on} - V_{R1}$

$= V_{in} - V_{D1, on} - I R_1$

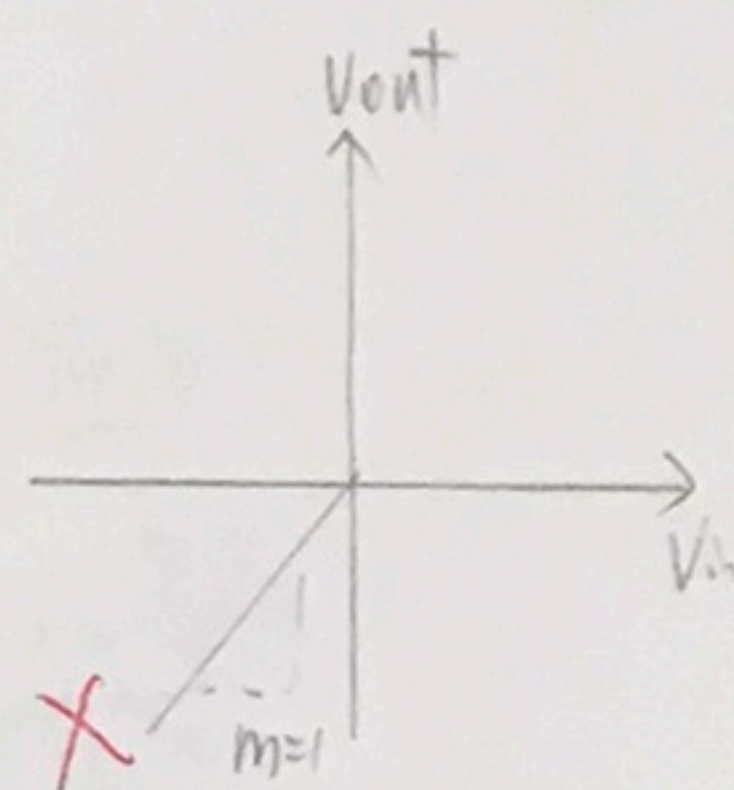

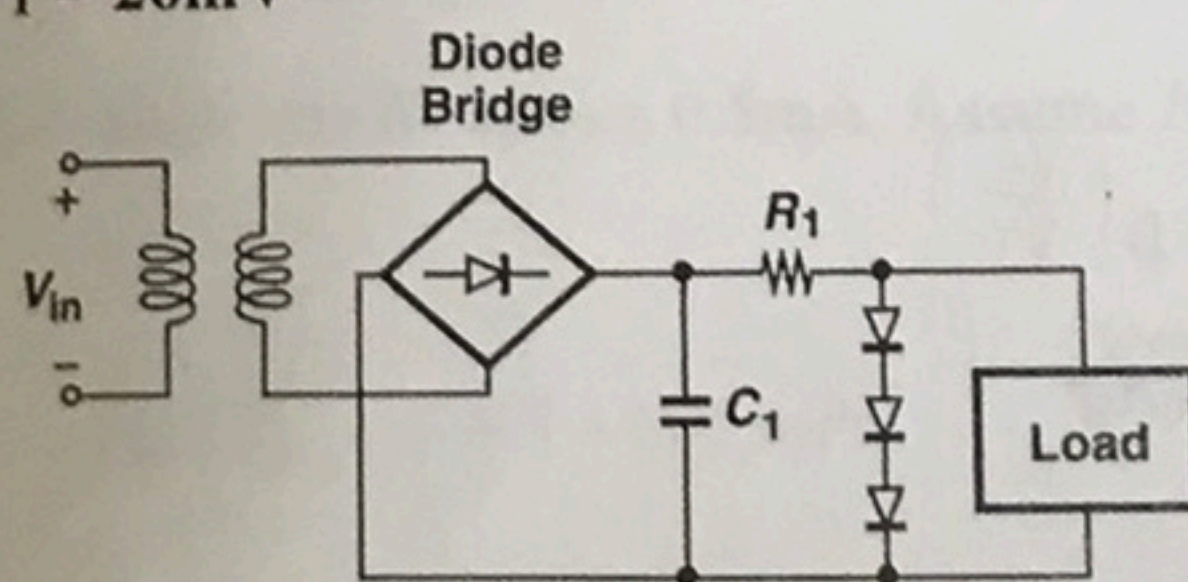6. (15%) Suppose the diodes carry a current of 5 mA and the load, a current of 20 mA. If the load current increases to 21 mA, what is the change in the total voltage across the three diodes? Assume R_I is much greater than $3r_d$. $r_d = V_T / I_D$, $V_T = 26$ mV





$$r_d = \frac{V_T}{I_D} = \frac{0.026}{5 \times 10^{-3}} = 5.2$$

$$\Delta V = (1 \times 10^{-3})(5.2 \times 3)$$

$$= 15.6 \times 10^{-3} \text{ V}$$

$$= 1.56 \times 10^{-2} \text{ V}$$

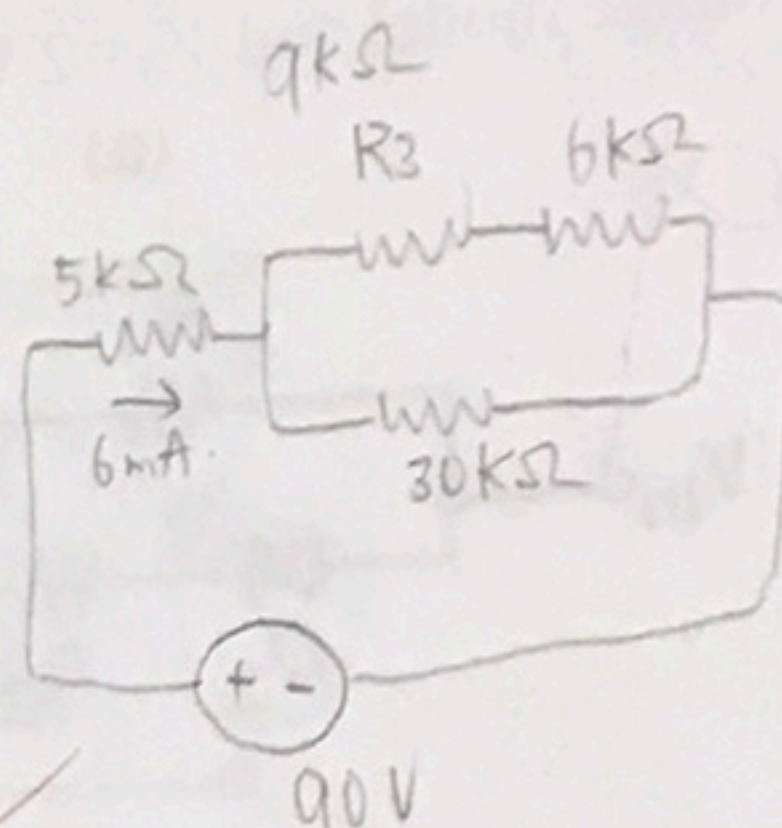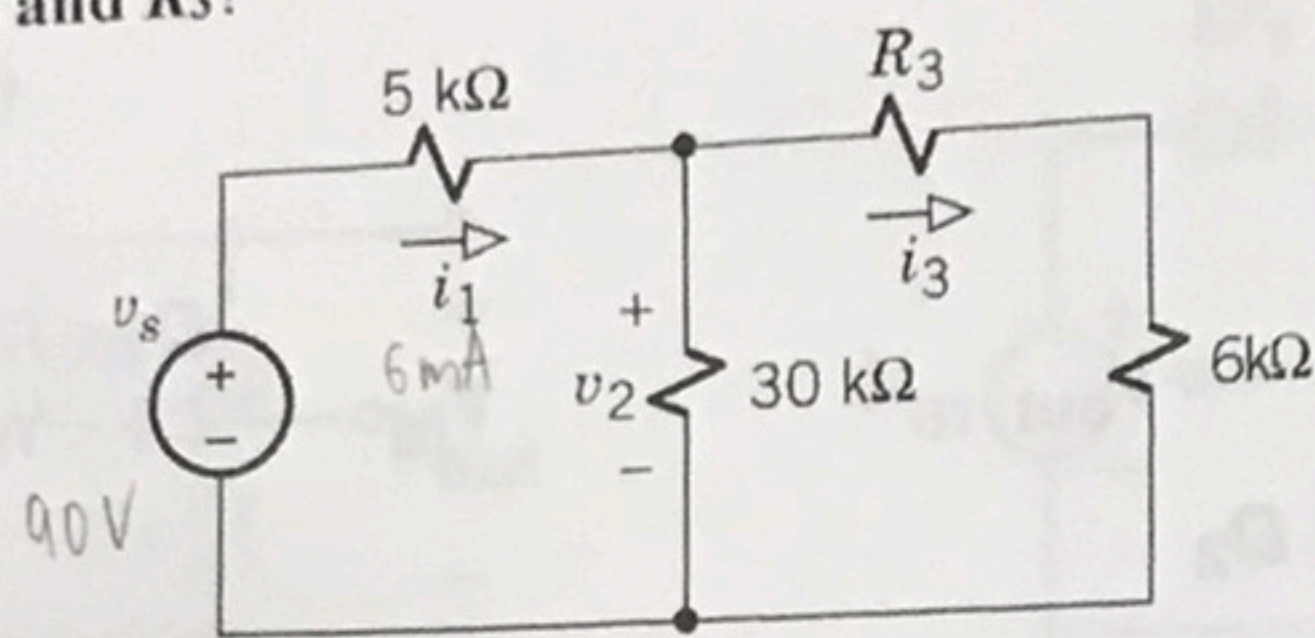7. (10%) If the circuit in the following figure represents a source and load with $v_s=90V$, and $i_1=6mA$, then what are the values of i_3 and R_3 ?



$$R_{th} = \frac{90}{6 \times 10^{-3}} = 15000 = 15k\Omega$$

$$R_3 : R_{L2} = 15 : 30 = 1 : 2$$

$$15 = 5 + \frac{1}{\frac{1}{R_3+6} + \frac{1}{30}}$$

$$\Rightarrow I_{R_3} : I_{V_2} = 2 : 1$$

$$\frac{1}{10} = \frac{1}{R_3+6} + \frac{1}{30}$$

$$i_3 = 6 \times \frac{2}{3} = 4mA \#$$

$$\frac{1}{10} = \frac{30+R_3+6}{(R_3+6)30}$$

$$360 + 10R_3 = 30R_3 + 180$$

$$20R_3 = 180$$

$$R_3 = 9k\Omega \#$$

8. (10%) Consider a pn junctions in forward bias. Initially a current of 5 mA flows through it, and the current increases by 8 times when the forward voltage is increased by 1.5 times. Determine the initial bias applied and reverse saturation current. ($V_T = 26mV$) $I_D = I_S \exp(V_D/V_T)$ $V_T = 26mV$

$$5 \times 10^{-3} = I_S \cdot \exp\left(\frac{V_0}{V_T}\right)$$

$$5 \times 10^{-3} = I_S \cdot e^{\frac{5 \times 10^{-3}}{0.026}}$$

$$I_S = \frac{5 \times 10^{-3}}{e^{\frac{5}{26}}}$$

+7

#

+2

