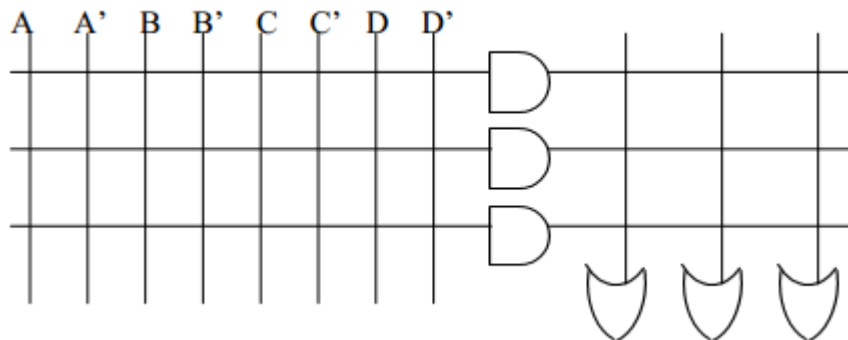


Chapter Exam

Appendix C-The Basics of Logic Design

2012/03/06

1. In Boolean algebra, there is a Consensus Theorem. Try to prove the following two equations are true. (20%)
 - i) $X \cdot Y + \sim X \cdot Z + Y \cdot Z = X \cdot Y + \sim X \cdot Z$
 - ii) $(X + Y) \cdot (\sim X + Z) = (Y + Z)$
2. Try to prove De Morgan's Laws using truth table. (20%)
 $A \cdot B \equiv \sim (\sim A + \sim B)$
 $A + B \equiv \sim (\sim A \cdot \sim B)$
3. Implement the function $F(A, B, C, D) = A \cdot B + (\sim C \cdot \sim D)$.
 - i) 2-input AND and OR gates and inverters. (5%)
 - ii) 2-input NAND gates. (5%)
 - iii) 2-input NOR gates. (5%)
 - iv) An AND/OR PLA. (10%)



4. What are the differences between combinational logics and sequential logics? (10%)
5. Draw a 1-bit full adder using 2 1-bit half adder in combination logic with the **input** a, b, carry_in and with the **output** sum, carry_out. (15%)
6. Using the result of (5) to briefly draw out 32-bit adder. (10%)